

NAME Kshitiz Thapa & Catherine Sarmiento
REPORT DATE November 15, 2018

COURSE ENGR 2730 Digital Logic
DUE DATE December 5, 2018
INSTRUCTOR: Shahram Rohani

Term Project Fall 2018

Finite State Machines in VHDL

| EVALUATION TOPIC | COMMENTS |
|-----------------------------|-----------------------|
| 1. Cover page | _____ |
| 2. Table of Contents | _____ |
| 3. Introduction | _____ |
| 4. Objectives | _____ |
| 5. Equipment | _____ |
| 6. Procedure | _____ |
| 7. Discussion of Results | _____ |
| 8. Analysis and Conclusions | _____ |
| 9. Supporting Documents | _____ |
| | Composite Score _____ |

EVALUATOR COMMENTS

Department of
Engineering Technology
ENGR 2730: Digital Logic Lab

Term Project Fall 2018
Finite State Machines in VHDL

 


TABLE OF CONTENTS

| | |
|-------------------------------|----|
| Introduction..... | 4 |
| Objectives..... | 5 |
| Equipment..... | 6 |
| Procedure..... | 7 |
| Discussion of Results..... | 9 |
| Analysis and Conclusions..... | 13 |
| Supporting Documents..... | 14 |

INTRODUCTION

The “Finite State Machines in VHDL” is a collaborative work to showcase the VHDL programming learned during the semester and how it applies to the abstract concept of Finite State Machines. The VHDL is programmed through Intel’s Quartus Pro Software with the use of Cyclone IV EP4CE115F29C7 Field Programmable Gate Array Integrated Circuit on a DE2-115 Altera Terasic board. With the use of VHDL, the goal is to program a simple traffic light circuit.

Traffic lights are signaling devices that control the flow of traffic and are very important to both pedestrians and vehicle drivers. Especially in big cities where there is a lot of congestion, traffic lights play an important role in saving time and ensuring road safety. Traffic light designs have evolved throughout the years, but recent designs feature the use of Red, Yellow and Green LED lights. Most traffic lights are programmed with a fixed cycle however modern traffic lights at metropolitan areas allow pedestrians to override and affect its operation.

Great emphasis is made to assure that our Traffic light design is in conjunction with the concepts of finite state machines. Finite state machines are defined as a system that follows a sequence of pre-defined states.

Hours were spent in the VHDL programming process to ensure the logical operation of the traffic light simulation on the Altera board. The state diagrams and figures provided were of great aid and helped the programmers in the design process.

This project emphasizes the use of road vehicle sensors in its design with the goal of improving traffic light systems operation which save vehicle operators waiting time. The project also aims to program the states with the correct logic to avoid collisions and to ensure the safety of drivers that depend heavily on the function of the road traffic light. The next sections will discuss the functionality and code structure of the traffic light simulation.

OBJECTIVES

The main objective of this project is to design a Traffic Light controller using the State Machines. We will be creating three VHDL files under this project with file names FSM, Traffic and Divider. The FSM is the VHDL file where we write the codes for different states of the traffic light progression and what the output is going to be in binary.

The Divider module is used to slow down the external clock input `CLOCK_50` from 50 MHz to 1 Hz. The Traffic module works as a tying module which connects the FSM and the Divider to the Altera board for code implementation.

The objective of the first part of the project is to implement a design of a traffic light at an intersection of Main Street (1) with Second Street (2). The traffic light controller should go through transitions to get 3 green clocks, 2 yellow clocks and 3 red clocks. This means that the project will transition through 8 total clocks before repeating.

For the objective of the second part of the project, sensors are added to the traffic control system. Whenever there is a car waiting in one of the streets and there is no car in the other street, the lights for the waiting car should turn green. This design is structured so that sole cars will not need to wait when the road is empty of incoming vehicles thus saving time.

For the objective of the third part of the project, special features will be added to the project i.e. Fire Truck Override and Night Time Override. As a general overview, the Fire Truck Override is a feature that detects the sensor which turns the lights to red to signal caution whenever there is an incoming fire truck .

A second feature incorporated in this design is a Night Time Override which is a state transition that keeps light blinking red to signal caution whenever there is some maintenance going on ahead or simply when lights do not run the regular cycle at night. The next section will discuss the equipment involved in the design of this project.

The biggest objective of the programmers is to make sure the logic is incorporated well into the code and that states progress to the next state correctly.

EQUIPMENT

Discussed below are the equipment used in this project along with their descriptions:

Quartus Prime Lite software

Intel® Quartus® Prime Design Software is a design software that includes everything needed to design for Intel FPGAs, SoCs, and CPLDs. This includes design entry, synthesis to optimization, verification, and simulation. Quartus dramatically increases capabilities on devices with multi-million logic elements, providing designers with an ideal platform for next-generation design opportunities. There are numerous versions of this software, but in this project, Intel Quartus Prime Lite was used. This software may also be utilized to create VHDL files and to translate codes for logic circuits. The software compiles the code and uploads the code to the Altera board.

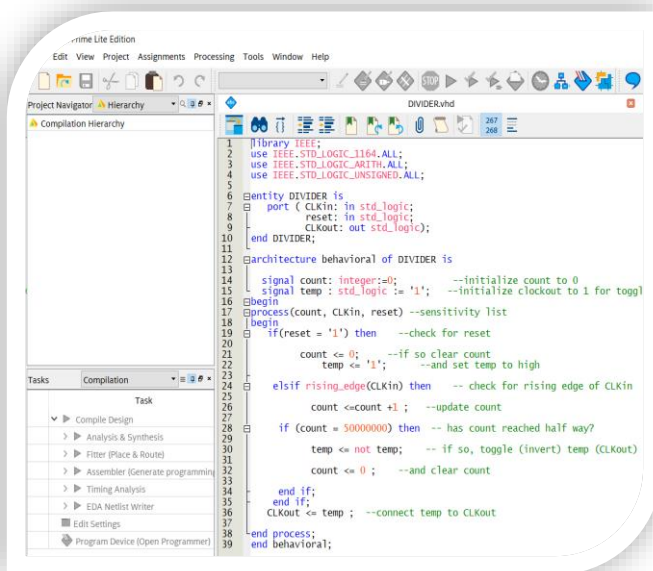


Figure 1: Intel Quartus Software

 


Figure 2: Altera DE2-115 Cyclone IV E Hardware

Altera DE2-115 Cyclone IV E hardware

Altera DE2-115 Cyclone IV E is the main hardware used in this project. The Altera logic board receives the written code from Quartus and in this simulation acts like a mini traffic light controller. The Cyclone IV E device equipped on the DE2-115 features 114,480 logic elements (LEs), the largest offered in the Cyclone IV E series, up to 3.9-Mbits of RAM, and 266 multipliers.

PROCEDURE

For Part I of the project, we first need to create a new Quartus II project in the software and name it as you want. Then , we need to create three new VHDL files within the project and name them Divider, FSM and Traffic respectively.

In the FSM module, we will declare a clock input variable and 8 different variables for 8 lighting condition(3 green, 2 yellow and 3 red) as a signal type. Then we can simply implement the traffic light as a form of 6 flip-flops using the case statement. The case statement will update the present state to the next state to result in change of lights. A With-Select statement is also used which defines and differentiates the different traffic light signal variable from each other. In the Divider module, we use some if-else statement to divide the clock input from 50 MHz to 1 Hz. In the Traffic module, two port map statement are written each for FSM and Divider module to tie together the written code with the logic board for real-time implementation.

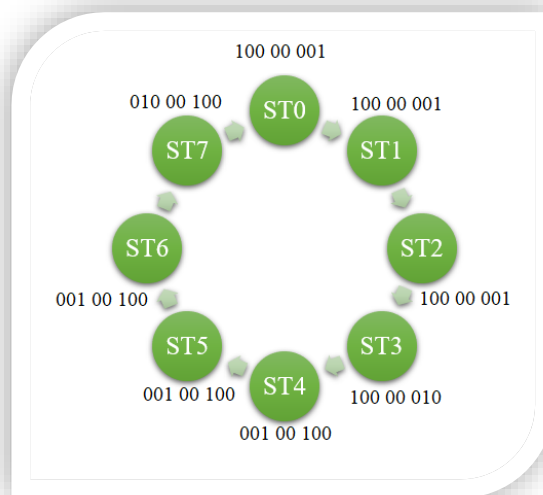


Figure 3: Finite State Diagram

For Part II of the project, changes will be made to the codes from Part I. Two switches SW(1) and SW(2) are used in the board as sensor which will detect if a car is waiting in one street. The Divider module is similar to preceding programs that have been worked in the class. In the FSM module, few if-else statements are used to implement the conditions when both are street have waiting cars(sensor is “11”), both don’t have any cars(sensor is “00”) or a car is waiting in one street(sensor is “01” or “10”).

In two conditions where both streets have cars, and none have waiting cars, (both switches high (11) or low (00) together), the system works and goes through the cycle shown in Figure 3 above. Whenever there is only one car waiting in one of the streets (means if only one of the switches is high (10 or 01)), the light on the car side is changed to green by updating the present state to next state using the case statement. The diagram in Figure 3 can be used to implement

the different sensor condition. For the Traffic module, two port map statements are written to tie together the variables in the VHDL file with the ports in the board with the help of Figure 2 given below.

 


Figure 4: Traffic Schematic Diagram

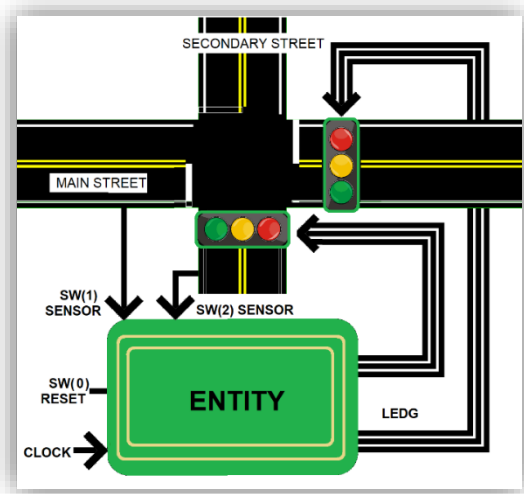


Figure 5: Entity Declarations and Case Statements

| A | Sensor1 | Sensor2 | Go where? |
|-------|---------|---------|---------------------|
| If | 0 | 0 | Move on to ST1 |
| If | 1 | 1 | Move on to ST1 |
| Elsif | 1 | 0 | Stay at green1: ST0 |
| else | | | Move on to ST3 |

| B | Sensor1 | Sensor2 | Go where? |
|-------|---------|---------|---------------------|
| If | 0 | 0 | Move on to ST5 |
| If | 1 | 1 | Move on to ST5 |
| Elsif | 0 | 1 | Stay at green1: ST4 |
| else | | | Move on to ST7 |

For Part III of the program, special features such as a fire truck override was programmed and activated whenever Switch 4 is on. The firetruck override turns the stoplights on Main Street and Second Street to red to signal caution. Intuitively the cars move to the right then stop.

Another feature of the Traffic Light project is a night time override or a maintenance status where the sensors take a break and just flash or blink Red until the Traffic Light is turned on the next morning. This feature is activated when Switch 5 is turned on.

DISCUSSION OF RESULTS

The states and signals were declared and once the initial code was written, the program was burned into the Altera Board. On the following pages are the codes and diagrams of the Finite State Machine progression results of the program:

```
if clk'event AND clk = '1' THEN
  if (sensor = "0000" or sensor = "0011") THEN
    case next_state IS
      when sT0 => next_state <= sT1;
      when sT1 => next_state <= sT2;
      when sT2 => next_state <= sT3;
      when sT3 => next_state <= sT4;
      when sT4 => next_state <= sT5;
      when sT5 => next_state <= sT6;
      when sT6 => next_state <= sT7;
      when sT7 => next_state <= sT0;
```

The initial state diagram features 7 states in which there are 3 counts of green lights, 2 yellows and 3 red state progressions. States 8 to 14 were added as it was needed in the special functionality of our traffic light simulation.

```
architecture Behavioural of FSM is
  type states IS (sT0, sT1, sT2, sT3, sT4, sT5, sT6, sT7, sT8, sT9, sT10, sT11, sT12, sT13, sT14);
  Signal next_state: states;
```

Two versions of the Simulation were programmed, one of which was a complex code which routes the output binary to the LEDR, LEDG and HEX output. LEDR representing red, LEDG representing green and lastly the HEX display representing the yellow light. Below is the result of the **complex** program that was written:

 


Figure 6: LED Output when an input of Switch 0001 or State 0, State 1, State 2 is activated

 


Figure 7: LED Output of Complex Code at State 3



Figure 8: Led Output when an input of Switch 0010 or State 4, State 5, State 6 is activated


 


Figure 9: LED Output of Complex Code at State 7

 On the next page is the result from the finite state machine progression of the **simple** code:



For the special feature, when switch 3 was on, the firetruck override was activated. Two case statements were coded that enabled a Firetruck Emergency function when a firetruck is approaching and a Night time override or maintenance mode switch that will put the lights on a Flashing red status. Switch 0 controls the reset function of the traffic light cycle. The two user special switches 3, 4 and its functionality is shown in the code below:



Figure 10: Led Output of Firetruck Override when an input of Switch 10XXX is activated

```
--FIRETRUCK OVERRIDE
if sensor = "0100" THEN
    next_state <= ST10;
end if;
```



Figure 11: LED Output of Night Time / maintenance mode when an input of Switch 1XXX is activated

```
--NIGHT TIME CAUTION
if sensor = "1000" THEN
    next_state <= ST8;
end if;|
```

The main difference between our simple and complex program was how the outputs were routed and how program was coded. Below is a snippet code of the simple version:

```
with next_state select OUTPUT <=
    "10000001" when ST0,
    "10000001" when ST1,
    "10000001" when ST2,
    "10000010" when ST3,
    "00100100" when ST4,
    "00100100" when ST5,
    "00100100" when ST6,
    "01000100" when ST7;
```

In the complex file, there were multiple outputs that led to either LEDG, LEDR, or HEX outputs. The design was intended to showcase innovation and creativity through representing the most accurate colors. On the next page is an overview of the complex program and how VHDL is effective at organizing codes and how readable it can be:

```

with next_state select RED <=
  "10000000" when ST0,
  "10000000" when ST1,
  "10000000" when ST2,
  "10000000" when ST3,
  "00000100" when ST4,
  "00000100" when ST5,
  "00000100" when ST6,
  "00000100" when ST7,

  "10000100" when ST8,
  "00000000" when ST9,

  "10000100" when ST10,
  "10000100" when ST11,
  "10000100" when ST12,
  "10000100" when ST13,
  "10000100" when ST14;

with next_state select GREEN <=
  "00000001" when ST0,
  "00000001" when ST1,
  "00000001" when ST2,
  "00000000" when ST3,
  "00100000" when ST4,
  "00100000" when ST5,
  "00100000" when ST6,
  "00000000" when ST7,

  "00000000" when ST8,
  "00000000" when ST9,

  "00000000" when ST10,
  "00000000" when ST11,
  "00000000" when ST12,
  "00000000" when ST13,
  "00000000" when ST14;

with next_state select YELLOW1 <=
  "11111111" when ST0,
  "11111111" when ST1,
  "11111111" when ST2,
  "10000000" when ST3,
  "11111111" when ST4,
  "11111111" when ST5,
  "11111111" when ST6,
  "11111111" when ST7,

  "11111111" when ST8,
  "11111111" when ST9,

  "11111111" when ST10,
  "11111111" when ST11,
  "11111111" when ST12,
  "11111111" when ST13,
  "11111111" when ST14;

with next_state select YELLOW2 <=
  "11111111" when ST0,
  "11111111" when ST1,
  "11111111" when ST2,
  "11111111" when ST3,
  "11111111" when ST4,
  "11111111" when ST5,
  "11111111" when ST6,
  "10000000" when ST7,

  "11111111" when ST8,
  "11111111" when ST9,

  "11111111" when ST10,
  "11111111" when ST11,
  "11111111" when ST12,
  "11111111" when ST13,
  "11111111" when ST14;

```

There are three modules in this project. The first module, FSM, contains the functionality of the traffic lights. Entities, architecture and signals are declared. The behavior of states, which is a cycle from 0 to 7, is declared in this section. The states will cycle repetitively until inputs are changed. The FSM module contains Case statements that signal how the lights should react in different input sensor scenarios. With select statements program how the outputs get routed to the LEDG, LEDR, and HEX displays when it is at a certain state.

The FSM and DIVIDER files are tied together in the third file, TRAFFIC. The ropes are tied, and the inputs and outputs are declared in this file. Each sub file played a great role in making sure the whole program runs. Programming in modules instead of doing one single file creates less errors and contributes to the easy readability of the program.

ANALYSIS AND CONCLUSIONS

Traffic Lights are important in ensuring safety on the road and are a great example of demonstrating how a finite state machine works. These machines go through a simple cycle with defined progressions depending on which state it is currently in.

Before starting the code, a great way to save time in programming projects is to strategize, do some planning, analyze diagrams and simplify the logic. Due to the limitations of the fixed LED arrangement, there was great difficulty in trying to accurately simulate a traffic light with the exact color and placement. There were plenty of ways to account for the circuit design differences between a Traffic Light Circuit versus an Altera Board and substitutions were done to represent the sensors and light colors. When all other groups stuck to the standard instruction of routing outputs to LEDG displays, our group wanted to incorporate some creativity in our design by routing the outputs to similarly colored displays such as LEDG, LEDR and HEX. This plan was successfully achieved and shown in the demonstration of our code.

The project “Finite State Machines on VHDL” focuses on the abstract concept of Finite State Automata and how they are incorporated in the design of Quartus Pro. Patterns occur frequently in nature and with the application of Finite State Machines, these repetitions can be simplified. The built in Finite State Machine feature in VHDL makes programming easier and faster.

Learning various examples throughout the semester have given students a preview of the countless logic designs that can be expressed through VHDL from adders, multiplexers, binary coded decimal counters etc. Traffic light variations like timed crosswalks, sensors, exclusive lefts, exclusive rights can be programmed easily with VHDL. VHDL is also very intuitive and similar to C++ so learning the language is easier to achieve.

Simplicity and easy usability are at the heart of Intel’s Quartus Pro. With VHDL programming, there is so much more that can be programmed, and programmers can relax, type less and save some time.

SUPPORTING DOCUMENTS

SIMPLE CODE VERSION I (All LEDG outputs used)

FSM.VHD

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  entity FSM is
7  Port(
8      Sensor    : IN std_logic_vector(2 downto 1);
9      reset      : IN std_logic;
10     clk        : IN std_logic;
11     OUTPUT     : OUT std_logic_vector(7 downto 0)
12 );
13 end FSM;
14
15 architecture Behavioural of FSM is
16     type states IS (ST0, ST1, ST2, ST3, ST4, ST5, ST6, ST7);
17     signal next_state: states;
18
19 begin
20     process( clk, sensor)
21     BEGIN
22         if clk'event AND clk = '1' THEN
23
24
25
26             if (sensor = "0000" or sensor = "0011") THEN
27
28                 case next_state IS
29                     when ST0 => next_state <= ST1;
30                     when ST1 => next_state <= ST2;
31                     when ST2 => next_state <= ST3;
32                     when ST3 => next_state <= ST4;
33                     when ST4 => next_state <= ST5;
34                     when ST5 => next_state <= ST6;
35                     when ST6 => next_state <= ST7;
36                     when ST7 => next_state <= ST0;
37
38                     end case;
39
40             elsif (reset ='1') then
41                 next_state <= ST0;
42
43             elsif sensor = "00001" THEN          -- CAR ON MAIN STREET
44
45
46                 if next_state = ST0 THEN          -- IF LIGHT IS ALREADY GREEN
47                     next_state <= ST0;          -- STAY GREEN
48
49                 elsif next_state = ST1 THEN          -- IF LIGHT IS ALREADY GREEN
50                     next_state <= ST0;          -- STAY GREEN
51
52                 elsif next_state = ST2 THEN          -- IF LIGHT IS ALREADY GREEN
53                     next_state <= ST0;          -- STAY GREEN
54
55                 elsif next_state = ST3 THEN          -- IF LIGHT IS ALREADY GREEN
56                     next_state <= ST0;          -- STAY GREEN
57
58                 elsif next_state = ST4 then          -- IF LIGHT IS RED ON MAIN STREET
59                     next_state <= ST7;          -- CAUTION BEFORE GREEN
60
61                 elsif next_state = ST5 then          -- IF LIGHT IS RED ON MAIN STREET
62                     next_state <= ST7;          -- CAUTION BEFORE GREEN
63
64                 elsif next_state = ST6 then          -- IF LIGHT IS RED ON MAIN STREET
65                     next_state <= ST7;          -- CAUTION BEFORE GREEN
66
67                 elsif next_state = ST7 then          -- IF LIGHT IS AT CAUTION
68                     next_state <= ST0;          -- MAKE IT GREEN
69
70             end if;
71
72
```

```

74 |         elsif sensor = "00010" THEN           -- CAR ON SECOND STREET
75 |
76 |
77 |             if next_state = ST0 THEN           -- IF LIGHT IS RED ON SECOND STREET
78 |                 next_state <= ST4;             -- CAUTION BEFORE GREEN LIGHT
79 |
80 |             elsif next_state = ST1 then        -- IF LIGHT IS RED ON SECOND STREET
81 |                 next_state <= ST4;             -- CAUTION BEFORE GREEN LIGHT
82 |
83 |             elsif next_state = ST2 then        -- IF LIGHT IS RED ON SECOND STREET
84 |                 next_state <= ST4;             -- CAUTION BEFORE GREEN LIGHT
85 |
86 |             elsif next_state = ST3 then        -- IF LIGHT IS CAUTION ON SECOND STREET
87 |                 next_state <= ST4;             -- CAUTION BEFORE GREEN LIGHT
88 |
89 |             elsif next_state = ST4 then        -- IF LIGHT IS ALREADY GREEN ON SECOND STREET
90 |                 next_state <= ST4;             -- GREEN ON SECOND STREET
91 |
92 |             elsif next_state = ST5 then        -- IF LIGHT IS ALREADY GREEN ON SECOND STREET
93 |                 next_state <= ST4;             -- CAUTION BEFORE GREEN
94 |
95 |             elsif next_state = ST6 then        -- IF LIGHT IS ALREADY GREEN ON SECOND STREET
96 |                 next_state <= ST7;             -- CAUTION BEFORE GREEN
97 |
98 |             elsif next_state = ST7 then        -- IF LIGHT IS AT CAUTION
99 |                 next_state <= ST4;             -- MAKE IT GREEN
100 |
101 |             end if;
102 |
103 |         end if;
104 |
105 |     end process;
106 |
107 |     with next_state select OUTPUT <=
108 |         "10000001" when ST0,                  -- RED ON MAIN STREET
109 |         "10000001" when ST1,                  -- RED ON MAIN STREET
110 |         "10000001" when ST2,                  -- RED ON MAIN STREET
111 |         "10000010" when ST3,                  -- RED ON MAIN STREET
112 |         "00100100" when ST4,                  -- RED ON SECOND STREET
113 |         "00100100" when ST5,                  -- RED ON SECOND STREET
114 |         "00100100" when ST6,                  -- RED ON SECOND STREET
115 |         "01000100" when ST7;                  -- RED ON SECOND STREET
116 |
117 |     end Behavioural;
118 |
119 |

```

TRAFFIC.VHD

```

1 | library IEEE;
2 | use IEEE.STD_LOGIC_1164.ALL;
3 | use IEEE.STD_LOGIC_ARITH.ALL;
4 | use IEEE.STD_LOGIC_UNSIGNED.ALL;
5 | entity traffic is
6 |     port (
7 |         SW      : IN std_logic_vector(2 downto 0);
8 |         clock_50 : IN std_logic;
9 |         LEDG    : OUT std_logic_vector(7 downto 0));
10 | end traffic;
11 | architecture behavioral of traffic is
12 |     signal rope1: std_logic;
13 |     begin
14 |         A1:
15 |         entity work.DIVIDER(behavioral)
16 |         port map(CLKIn => CLOCK_50, reset => SW(0), CLKOut => rope1);
17 |         A2:
18 |         entity work.FSM(Behavioural)
19 |         port map(clk=> rope1, OUTPUT => LEDG, reset => Sw(0), sensor => SW(2 downto 1));
20 |
21 |     end behavioral;
22 |
23 |
24 |

```

COMPLEX CODE VERSION II (LEDG, LEDR, and HEX outputs)

TRAFFIC.VHD

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5  entity traffic is
6  port ( SW      : IN std_logic_vector(4 downto 0);
7        clock_50 : IN std_logic;
8        LEDG     : OUT std_logic_vector(7 downto 0);
9        HEX0     : OUT STD_LOGIC_VECTOR(6 downto 0);
10       HEX1     : OUT STD_LOGIC_VECTOR(6 downto 0);
11       LEDR     : OUT std_logic_vector(7 downto 0));
12
13 end traffic;
14 architecture behavioral of traffic is
15   signal rope1: std_logic;
16   begin
17     A1:
18     entity work.DIVIDER(behavioral)
19     port map(CLKIn => CLOCK_50, reset => SW(0), CLKout => rope1);
20     A2:
21     entity work.FSM(Behavioural)
22     port map(c1k=> rope1, GREEN => LEDG, RED => LEDR, YELLOW2 => HEX1, YELLOW1 => HEX0, reset => Sw(0), sensor => SW(4 downto 1));
23
24   end behavioral;
25
```

DIVIDER.VHD

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  entity DIVIDER is
7  port ( CLKin: in std_logic;
8        reset: in std_logic;
9        CLKout: out std_logic);
10 end DIVIDER;
11
12 architecture behavioral of DIVIDER is
13   signal count: integer:=0;      --initialize count to 0
14   signal temp : std_logic := '1'; --initialize clockout to 1 for toggle
15   begin
16     process(count, CLKin, reset) --sensitivity list
17     begin
18       if(reset = '1') then      --check for reset
19         count <= 0;             --if so clear count
20         temp <= '1';           --and set temp to high
21       elsif rising_edge(CLKin) then -- check for rising edge of CLKin
22         count <= count +1 ;     --update count
23       if (count = 50000000) then -- has count reached half way?
24         temp <= not temp;      -- if so, toggle (invert) temp (CLKout)
25         count <= 0 ;          --and clear count
26       end if;
27     end if;
28     CLKout <= temp ;           --connect temp to CLKout
29   end process;
30 end behavioral;
31
```


FSM.VHD

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  entity FSM is
7  Port(
8      Sensor      : IN std_logic_vector(4 downto 1);
9      reset       : IN std_logic;
10     clk         : IN std_logic;
11     GREEN       : OUT std_logic_vector(7 downto 0);
12     YELLOW1     : OUT STD_LOGIC_VECTOR(6 downto 0);
13     YELLOW2     : OUT STD_LOGIC_VECTOR(6 downto 0);
14     RED         : OUT std_logic_vector(7 downto 0);
15 );
16 end FSM;
17
18 architecture Behavioural of FSM is
19     type states IS (ST0, ST1, ST2, ST3, ST4, ST5, ST6, ST7, ST8, ST9, ST10, ST11, ST12, ST13, ST14);
20     signal next_state: states;
21
22 begin
23     process( clk, sensor)
24     BEGIN
25         if clk'event AND clk = '1' THEN
26
27
28
29             if (sensor = "0000" or sensor = "0011") THEN
30
31                 case next_state IS
32                     when ST0 => next_state <= ST1;
33                     when ST1 => next_state <= ST2;
34                     when ST2 => next_state <= ST3;
35                     when ST3 => next_state <= ST4;
36                     when ST4 => next_state <= ST5;
37                     when ST5 => next_state <= ST6;
38                     when ST6 => next_state <= ST7;
39                     when ST7 => next_state <= ST0;
40
41                     when ST8 => next_state <= ST9;    --NIGHT TIME CAUTION
42                     when ST9 => next_state <= ST8;    --NIGHT TIME CAUTION
43
44                     when ST10 => next_state <= ST11; --FIRETRUCK OVER RIDE
45                     when ST11 => next_state <= ST12; --FIRETRUCK OVER RIDE
46                     when ST12 => next_state <= ST13; --FIRETRUCK OVER RIDE
47                     when ST13 => next_state <= ST14; --FIRETRUCK OVER RIDE
48                     when ST14 => next_state <= ST7;
49
50                 end case;
51
52             elsif (reset ='1') then
53                 next_state <= ST0;
54
55
56                 --FIRETRUCK OVERRIDE
57             elsif sensor = "00100" THEN
58                 next_state <= ST10;    -- STAY RED UNTIL APPROPRIATE SENSOR IS ACTIVATED
59
60                 --NIGHT TIME CAUTION
61             elsif sensor = "10000" THEN
62                 next_state <= ST8;    -- BLINK NIGHT TIME LIGHTS WHEN ITS SWITCH 5
63
64             elsif sensor = "00001" THEN
65                 -- CAR ON MAIN STREET
66
67                 if next_state = ST0 THEN
68                     next_state <= ST0;    -- IF LIGHT IS ALREADY GREEN
69                     -- STAY GREEN
70
71                 elsif next_state = ST1 THEN
72                     next_state <= ST0;    -- IF LIGHT IS ALREADY GREEN
73                     -- STAY GREEN
74
75                 elsif next_state = ST2 THEN
76                     next_state <= ST0;    -- IF LIGHT IS ALREADY GREEN
77                     -- STAY GREEN
78
79                 elsif next_state = ST3 THEN
80                     next_state <= ST0;    -- IF LIGHT IS ALREADY GREEN
81                     -- STAY GREEN
82
83                 elsif next_state = ST4 then
84                     next_state <= ST7;    -- IF LIGHT IS RED ON MAIN STREET
85                     -- CAUTION BEFORE GREEN

```

```

81
82
83     elsif next_state = ST5 then -- IF LIGHT IS RED ON MAIN STREET
84         next_state <= ST7;      -- CAUTION BEFORE GREEN
85
86     elsif next_state = ST6 then -- IF LIGHT IS RED ON MAIN STREET
87         next_state <= ST7;      -- CAUTION BEFORE GREEN
88
89     elsif next_state = ST7 then -- IF LIGHT IS AT CAUTION
90         next_state <= ST0;      -- MAKE IT GREEN
91
92 end if;
93
94 elsif sensor = "00010" THEN    -- CAR ON SECOND STREET
95
96
97     if next_state = ST0 THEN    -- IF LIGHT IS RED ON SECOND STREET|
98         next_state <= ST4;      -- CAUTION BEFORE GREEN LIGHT
99
100    elsif next_state = ST1 then  -- IF LIGHT IS RED ON SECOND STREET
101        next_state <= ST4;      -- CAUTION BEFORE GREEN LIGHT
102
103    elsif next_state = ST2 then  -- IF LIGHT IS RED ON SECOND STREET
104        next_state <= ST4;      -- CAUTION BEFORE GREEN LIGHT
105
106    elsif next_state = ST3 then  -- IF LIGHT IS CAUTION ON SECOND STREET
107        next_state <= ST4;      -- CAUTION BEFORE GREEN LIGHT
108
109    elsif next_state = ST4 then  -- IF LIGHT IS ALREADY GREEN ON SECOND STREET
110        next_state <= ST4;      -- GREEN ON SECOND STREET
111
112    elsif next_state = ST5 then  -- IF LIGHT IS ALREADY GREEN ON SECOND STREET
113        next_state <= ST4;      -- CAUTION BEFORE GREEN
114
115    elsif next_state = ST6 then  -- IF LIGHT IS ALREADY GREEN ON SECOND STREET
116        next_state <= ST7;      -- CAUTION BEFORE GREEN
117
118    elsif next_state = ST7 then  -- IF LIGHT IS AT CAUTION
119        next_state <= ST4;      -- MAKE IT GREEN
120
121
122
123 --     else
124 --         next_state <= ST8;
125
126 end if;
127
128 end if;
129
130 end process;
131
132 with next_state select RED <=
133     "10000000" when ST0,      -- RED ON MAIN STREET
134     "10000000" when ST1,      -- RED ON MAIN STREET
135     "10000000" when ST2,      -- RED ON MAIN STREET
136     "10000000" when ST3,      -- RED ON MAIN STREET
137     "00000100" when ST4,      -- RED ON SECOND STREET
138     "00000100" when ST5,      -- RED ON SECOND STREET
139     "00000100" when ST6,      -- RED ON SECOND STREET
140     "00000100" when ST7,      -- RED ON SECOND STREET
141
142     "10000100" when ST8,      -- FLASH RED LIGHTS ON AT NIGHT
143     "00000000" when ST9,      -- FLASH RED LIGHTS OFF AT NIGHT
144
145     "10000100" when ST10,     -- STAY RED ON FIRETRUCK OVERRIDE
146     "10000100" when ST11,     -- STAY RED ON FIRETRUCK OVERRIDE
147     "10000100" when ST12,     -- STAY RED ON FIRETRUCK OVERRIDE
148     "10000100" when ST13,     -- STAY RED ON FIRETRUCK OVERRIDE
149     "10000100" when ST14;     -- STAY RED ON FIRETRUCK OVERRIDE
150

```



```

151 with next_state select GREEN <=
152     "00000001" when ST0,      -- GREEN ON SECOND STREET
153     "00000001" when ST1,      -- GREEN ON SECOND STREET
154     "00000001" when ST2,      -- GREEN ON SECOND STREET
155     "00000000" when ST3,      -- CAUTION ON SECOND STREET
156     "00100000" when ST4,      -- GREEN ON MAIN STREET
157     "00100000" when ST5,      -- GREEN ON MAIN STREET
158     "00100000" when ST6,      -- GREEN ON MAIN STREET
159     "00000000" when ST7,      -- CAUTION ON MAIN STREET
160
161     "00000000" when ST8,      -- FLASH RED LIGHT ON AT NIGHT
162     "00000000" when ST9,      -- FLASH RED LIGHTS OFF AT NIGHT
163
164     "00000000" when ST10,     -- GREEN OFF ON FIRETRUCK OVERRIDE
165     "00000000" when ST11,     -- GREEN OFF ON FIRETRUCK OVERRIDE
166     "00000000" when ST12,     -- GREEN OFF ON FIRETRUCK OVERRIDE
167     "00000000" when ST13,     -- GREEN OFF ON FIRETRUCK OVERRIDE
168     "00000000" when ST14;     -- GREEN OFF ON FIRETRUCK OVERRIDE
169
170 with next_state select YELLOW1 <=
171
172     "1111111" when ST0,      -- yellow caution off
173     "1111111" when ST1,      -- yellow caution off
174     "1111111" when ST2,      -- yellow caution off
175     "1000000" when ST3,      -- CAUTION ON SECOND STREET
176     "1111111" when ST4,      -- yellow caution off
177     "1111111" when ST5,      -- yellow caution off
178     "1111111" when ST6,      -- yellow caution off
179     "1111111" when ST7,      -- yellow caution off
180
181     "1111111" when ST8,      -- CAUTION off FLASH RED LIGHTS ON AT NIGHT
182     "1111111" when ST9,      -- CAUTION off FLASH RED LIGHT OFF AT NIGHT
183
184     "1111111" when ST8,      -- CAUTION off FLASH RED LIGHTS ON AT NIGHT
185     "1111111" when ST9,      -- CAUTION off FLASH RED LIGHT OFF AT NIGHT
186
187     "1111111" when ST10,     -- CAUTION off STAY RED ON FIRETRUCK OVERRIDE
188     "1111111" when ST11,     -- CAUTION off STAY RED ON FIRETRUCK OVERRIDE
189     "1111111" when ST12,     -- CAUTION off STAY RED ON FIRETRUCK OVERRIDE
190     "1111111" when ST13,     -- CAUTION off STAY RED ON FIRETRUCK OVERRIDE
191     "1111111" when ST14;     -- CAUTION off STAY RED ON FIRETRUCK OVERRIDE
192
193 with next_state select YELLOW2 <=
194
195     "1111111" when ST0,      -- yellow caution off
196     "1111111" when ST1,      -- yellow caution off
197     "1111111" when ST2,      -- yellow caution off
198     "1111111" when ST3,      -- yellow caution off
199     "1111111" when ST4,      -- yellow caution off
200     "1111111" when ST5,      -- yellow caution off
201     "1000000" when ST6,      -- CAUTION ON MAIN STREET
202
203     "1111111" when ST8,      -- CAUTION off FLASH RED LIGHTS ON AT NIGHT
204     "1111111" when ST9,      -- CAUTION off FLASH RED LIGHT OFF AT NIGHT
205
206     "1111111" when ST10,     -- CAUTION off STAY RED ON FIRETRUCK OVERRIDE
207     "1111111" when ST11,     -- CAUTION off STAY RED ON FIRETRUCK OVERRIDE
208     "1111111" when ST12,     -- CAUTION off STAY RED ON FIRETRUCK OVERRIDE
209     "1111111" when ST13,     -- CAUTION off STAY RED ON FIRETRUCK OVERRIDE
210     "1111111" when ST14;     -- CAUTION off STAY RED ON FIRETRUCK OVERRIDE
211
212 end Behavioural;

```